

MINI (CLONE) PCB

LAST UPDATE: July 19, 2023

DISCLAIMER: I am not responsible for any harm or injury or even fatality that may arise from the building and usage of this device/PCB.


BUILD OF MATERIALS		
<i>Capacitors</i> C1 10u C2 1n C3 220n C4 1u C5 10u C6 1u C7 10u C9 15n C13 100n C14 1u C15 220u <i>Diodes</i> D1 LED D100 1N5817	<i>Semiconductors</i> Q2 J201 Q3 2N5457 Q4 J201 Q6 2N5089 <i>Resistors</i> R1 1m R2 47k R3 1m R4 1k R5 1k R6 33k R7 4k7 R8 1k R9 4k7 R10 1k R11 1k R15 1k R23 10R R25 4k7 RLED 3K3	<i>Potentiometers</i> TREBLE B10K GAIN B100K (dual gang) VOL A100K BASS C1M BIAS B10K TRIM1 50k TRIM2 10-20k TRIM3 50k

Notes:

- JFETS
 - Knowledge of biasing and/or selecting JFETs is **HIGHLY RECOMMENDED** and use of SMT JFETs is **HIGHLY RECOMMENDED**.
 - Depending on what JFETs are used (model, specs, etc.), you may need to alter the source resistor (Rs). I recommend socketing R4, R8, and R10. From my own experience, biasing Q3 and finding the appropriate source resistor (R8) is imperative to gain the full potential of the Bias knob.
 - There is a difference in the schematic JFETs and BOM due to the variance in reports about these parts. For example, in Gray Bench's analysis of the pedal, he identified the pedal had three 2N5457 JFETs for Q2, Q3, Q4. In some schematics like Effects Layouts' Liliput, Q2 and Q4 are J201 and Q3 is 2N5457. My builds match the similar JFET choice of Effects Layouts. Furthermore, if you use 2N5457, you will need R4, R8, and R10 accordingly because of the variance in Rs.
- Trimmers
 - Different schematics contain varying values for the trimmers. I personally use 50K in all my builds.
- Bias Knob
 - Preface that there is a Bias knob and there is the action of biasing a JFET's drain voltage.
 - To adjust Q3, the gain stage associated with the Bias knob, set the Bias to noon (50% wiper). Use TRIM2 to bias the drain voltage of Q3 to 4.5V. When turning the Bias knob, your drain voltage should change between 2 to 7V. If the knob does not work, you can either try to adjust the source resistor (make it higher or even lower).
 - If this does not work, you may need to try out another JFET from your supply pile. In my experience (anecdotal), one out of ten of my 2N5457s will not react correctly to the Bias knob.

- Pot Selection

- For Gain, B100K dual-gang potentiometer was noted in the initial schematic posted on an online forum and corroborated by the initial creator himself. However, Gray Bench noted it is an A100K dual-gang potentiometer in his analyzed model.
- For Bass, C500K was noted in the initial schematic posted on an online forum and corroborated by the initial creator himself. However, Gray Bench noted it is a C1M potentiometer in his analyzed model.

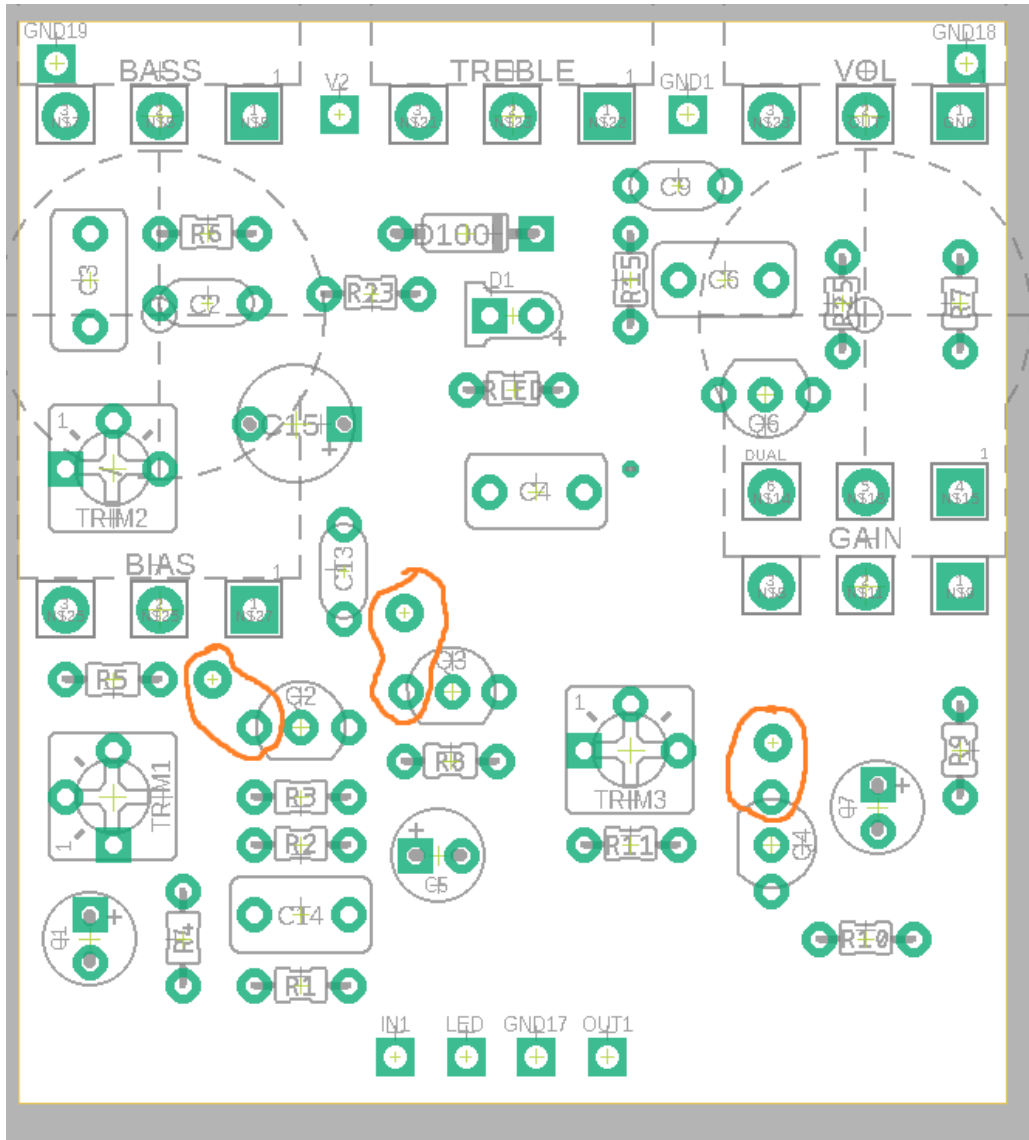


Bias all the drain voltages as follows:

- Q2 = 5.1 V +/- 0.2V
- Q3 = 4.5 V (adjust while Bias knob is 0:00)
 - Q4 = 4.5-4.7V


(I personally do 4.5V for all of these.)

You can use the empty pads to place a multimeter probe. The circles show which respective drain pin applies to each empty pad.


Schematic

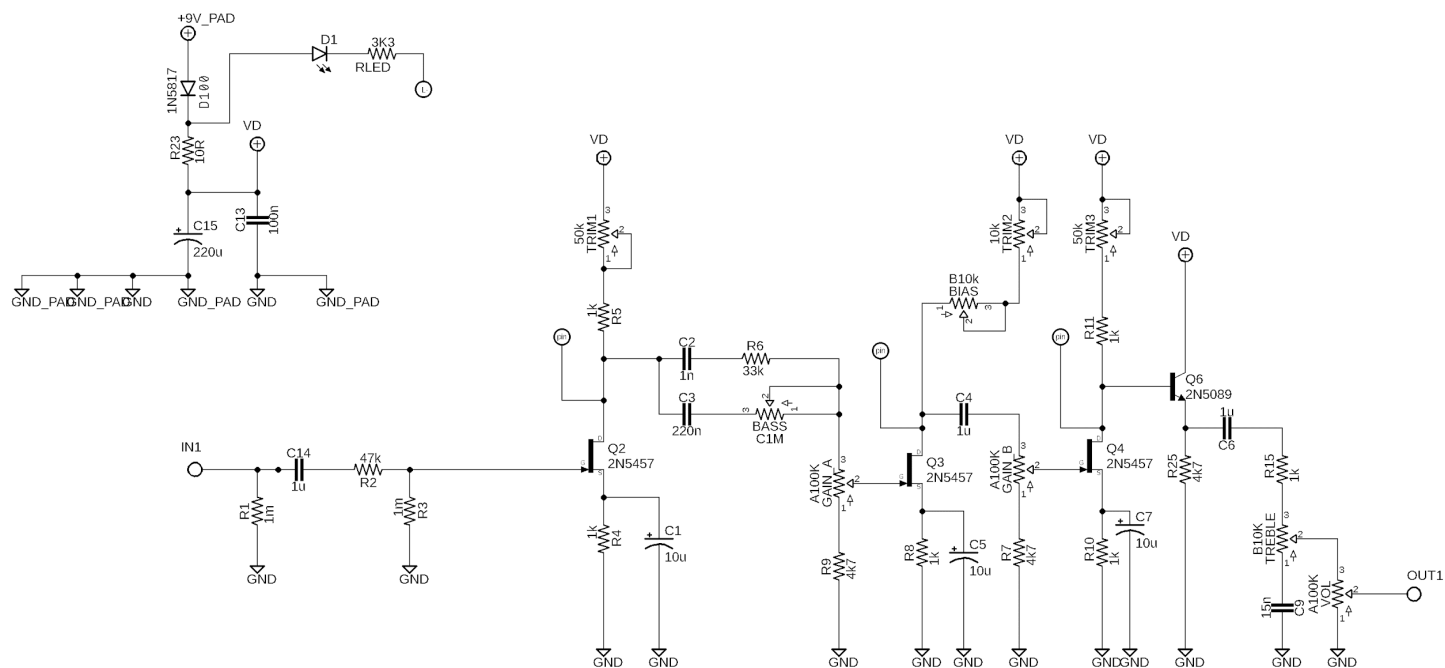

Wiring Diagram

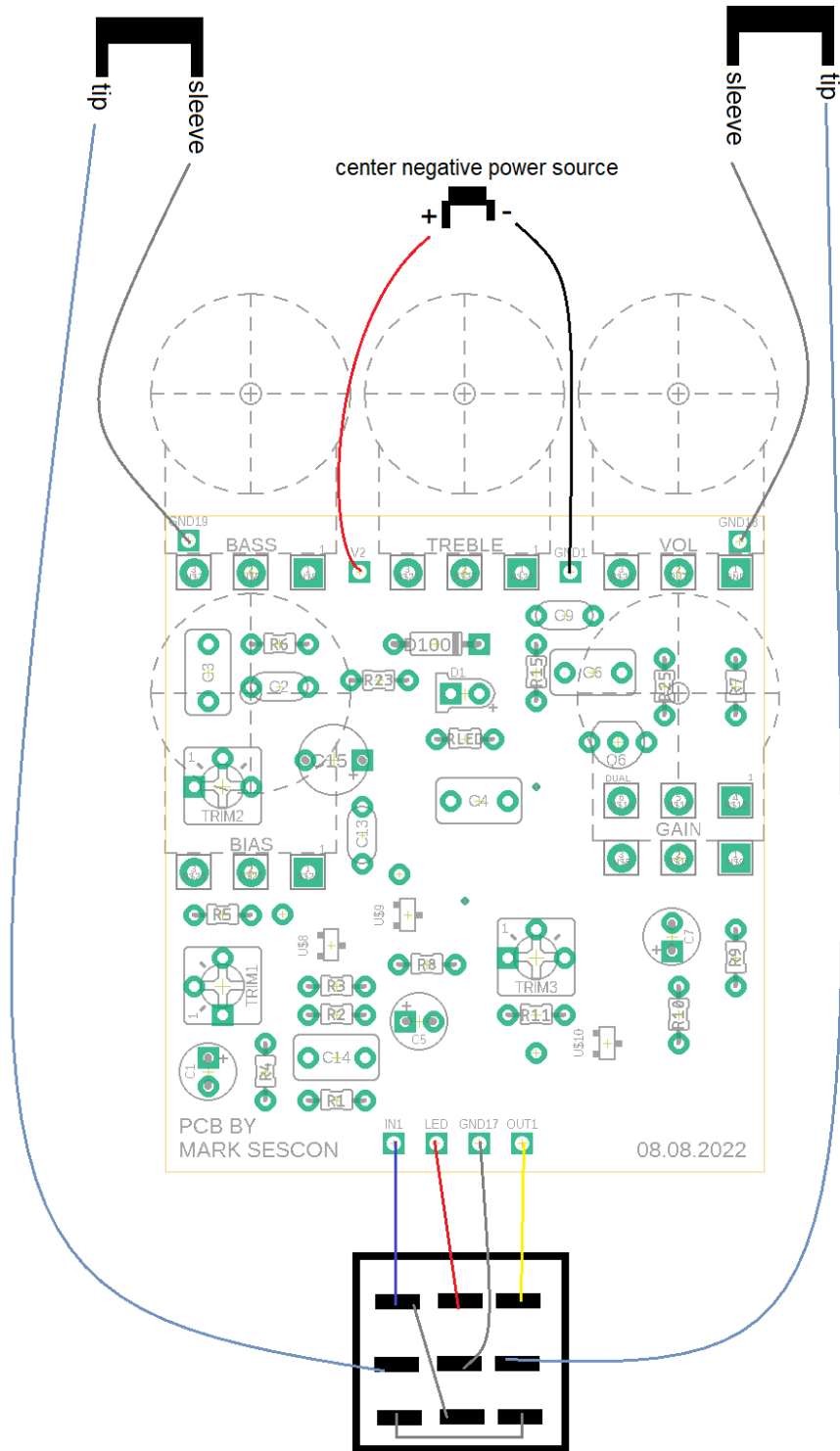

Proposed Drilling Template

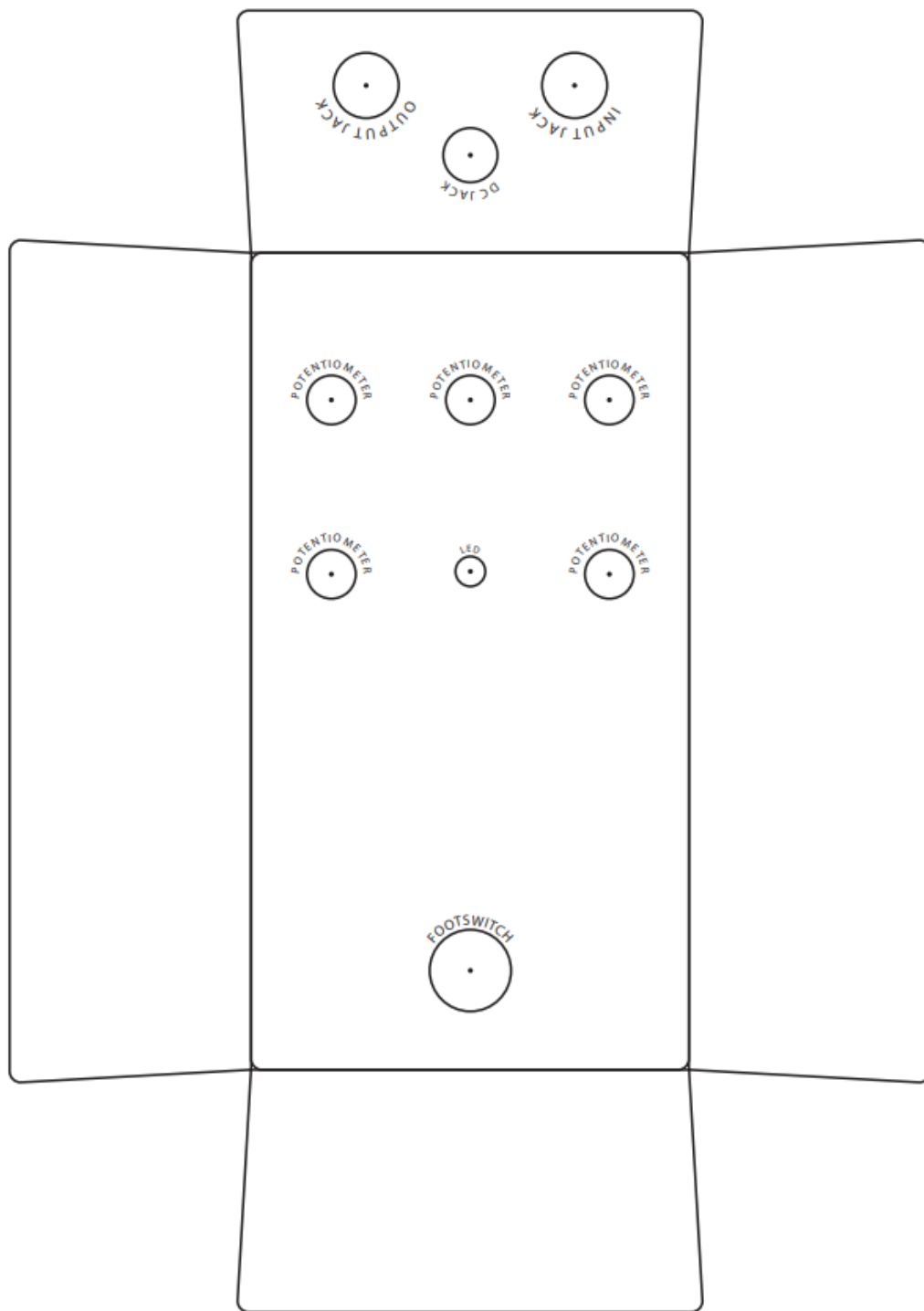

DO NOT PRINT THIS OUT AS A DRILLING TEMPLATE. It's meant to be a frame of reference for the *new* PCB layout. Please reference page 5 of this template:
<https://docs.pedalpcb.com/project/BayonetFuzz.pdf><https://docs.pedalpcb.com/project/6BandEQ-Potentiometer.pdf>.

Be mindful of the LED placement.

Additional Reading:

- Adjusting trimmer of Q3 in light of Bias and the source resistor (R8):
<https://www.freestompboxes.org/viewtopic.php?t=30921>
- Biasing JFETs: <http://diy.smallbearelec.com/HowTos/BreadboardBareAss/BreadboardBareAss.htm>
- Brian commenting with insight:
<http://tagboardeffects.blogspot.com/2016/07/smallsoundbigsound-mini-overdrive.html>
- Run Off Groove insight on JFETs:
<http://www.runoffgroove.com/fetzervalue.html>

Release Notes

- 2022
 - August 15 - Initial draft.
 - August 21 - Additional instructions about biasing JFETs. Additional instructions about Gain pot selection.
 - August 29 - Additional information about JFET and potentiometer selection. Additional information about how to adjust Bias knob. Wiring diagram.
- 2023
 - May 10 - I have since updated the PCB to accommodate the six knob configuration on Tayda and PedalPCB. No changes to the schematic have been made but some traces have been redone to accommodate this new layout. Included in this BOM is a proposed drill template that references page 5 of this template:
<https://docs.pedalpcb.com/project/BayonetFuzz.pdf><https://docs.pedalpcb.com/project/6BandEQ-Potentiometer.pdf>. Be mindful of the LED placement.
 - Background: The original PCB is meant to fit in the six knob configuration as proposed by Tayda and PedalPCB. Unfortunately, the spacing of the potentiometers was NOT correct. The original PCB will fit into the six knob configuration on Tayda and PedalPCB but will require the potentiometer legs be bent slightly (0.05 millions of an inch).
 - July - Updated schematic picture and provided additional information about adjusting the drain voltage for Q3. I have come to find that many people are having issues with the Bias knob “not working,” but the solution is quite straightforward albeit does require some cognizance on behalf of the builder.